

## Homework 2

(1) The input voltage  $U = 10 \sin(\omega t)$  V, draw the output waveforms of  $V$  in the circuits shown in Figure: (1a) and (1b). The diodes are modelled with a constant voltage drop model with  $e_{fd} = 0.7$  V.

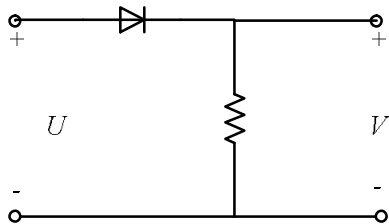


Figure: (1a)

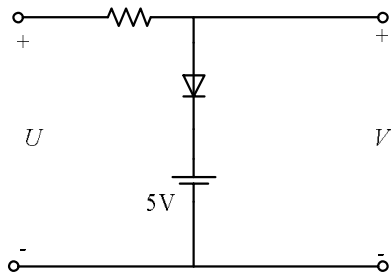


Figure: (1b)

(2) Determine  $V$  and  $I_A$ ,  $I_B$ ,  $I_C$  in the following circuit when

(a)  $U_A = U_B = 0$

(b)  $U_A = 4\text{V}, U_B = 0$

(c)  $U_A = U_B = 4\text{V}$

The diodes are ideal.

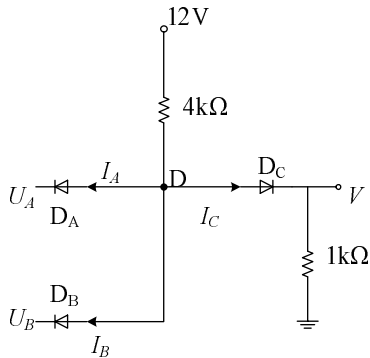


Figure: 2

(3) Draw the transfer characteristics ( $U$  versus  $V$ ) for the circuits shown below.  $U$  is the input voltage and  $V$  is the output voltage. The diodes are modelled with a constant voltage drop model with  $e_{fd} = 0.7$  V.

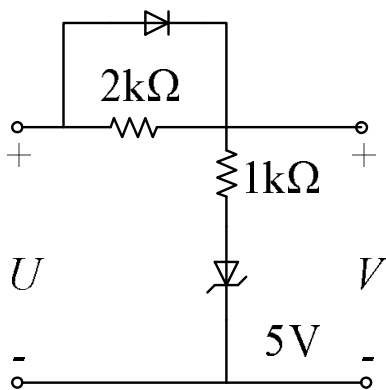


Figure: (3a)

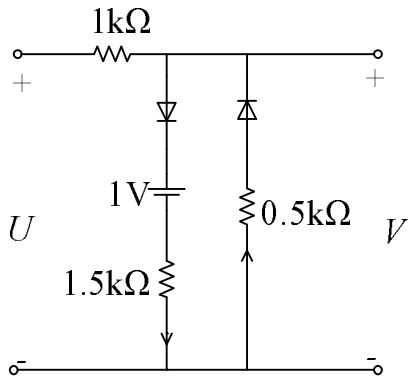


Figure: (3b)