

- For the common-emitter characteristics of Fig. 3.13, find the dc beta at an operating point of $V_{CE} = 8 \text{ V}$ and $I_C = 2 \text{ mA}$.
- Find the value of α corresponding to this operating point.
- At $V_{CE} = 8 \text{ V}$, find the corresponding value of I_{CEO} .
- Calculate the approximate value of I_{CBO} using the dc beta value obtained in part (a).

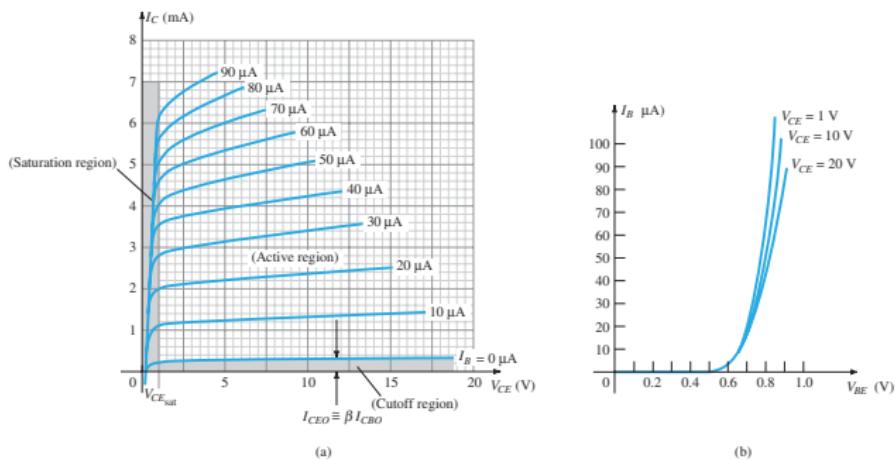


FIG. 3.13

2

Given the information provided in Fig. 4.123, determine:

- a. R_C .
- b. R_E .
- c. R_B .
- d. V_{CE} .
- e. V_B .

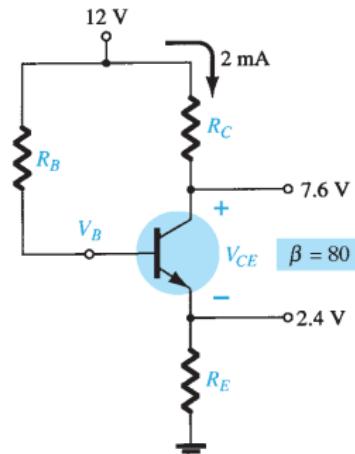


FIG. 4.123

3

For the networks of Fig. 5.164 and Fig. 5.165 :

- Determine $r_e = \frac{26 \text{ mV}}{I_E}$.
- Find Z_i and Z_o .
- Calculate A_v .

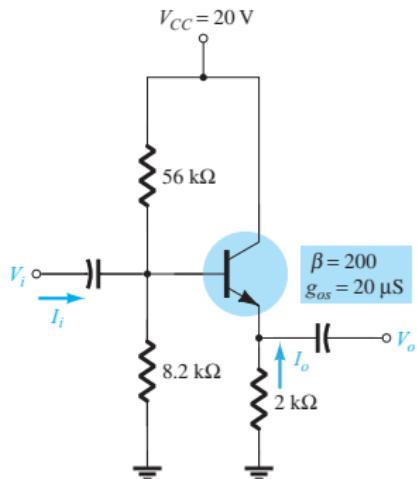


FIG. 5.164

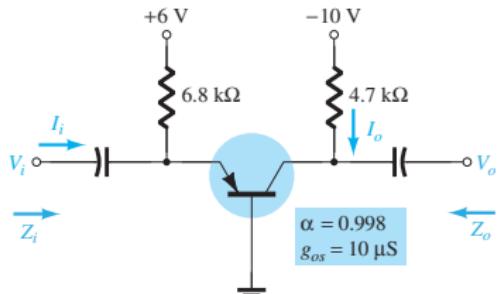


FIG. 5.165

For the networks of Fig. 9.80 and Fig. 9.81:

a. Determine $r_e = \frac{26 \text{ mV}}{I_E}$.

b. Find $A_{v_{mid}} = \frac{V_o}{V_i}$.

c. Calculate Z_i .

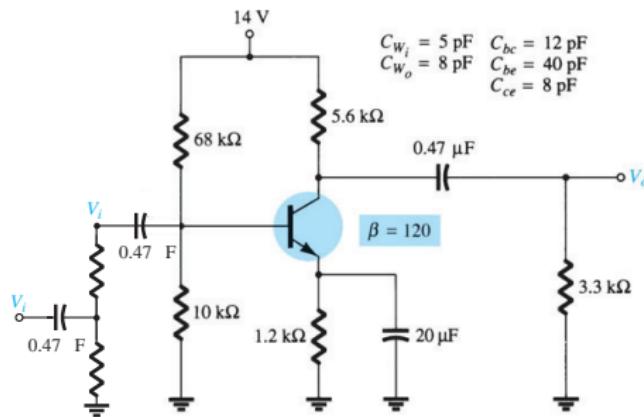


FIG. 9.80

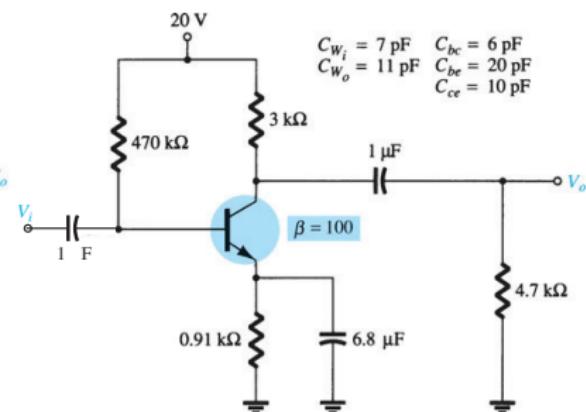


FIG. 9.81

If the input voltage to the power amplifier of Fig. 12.36 is 8-V rms, for the networks of Fig. 12.36 and Fig. 12.37, calculate:

- $P_o(ac)$.
- $P_i(dc)$.
- $\% \eta$.
- Power dissipated by both output transistors.

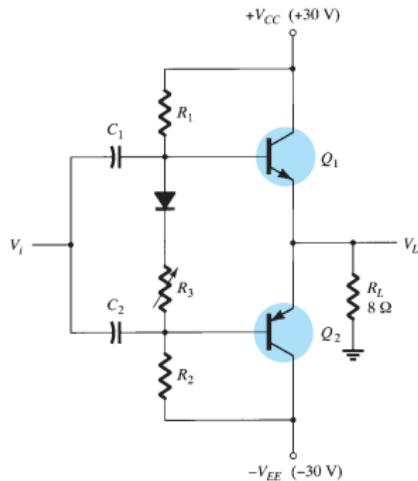


FIG. 12.36

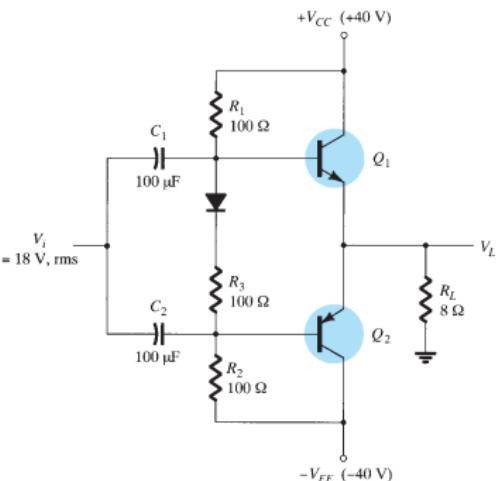


FIG. 12.37