

Calculate the output voltages V_2 and V_3 in the circuit of Fig. 10.72.

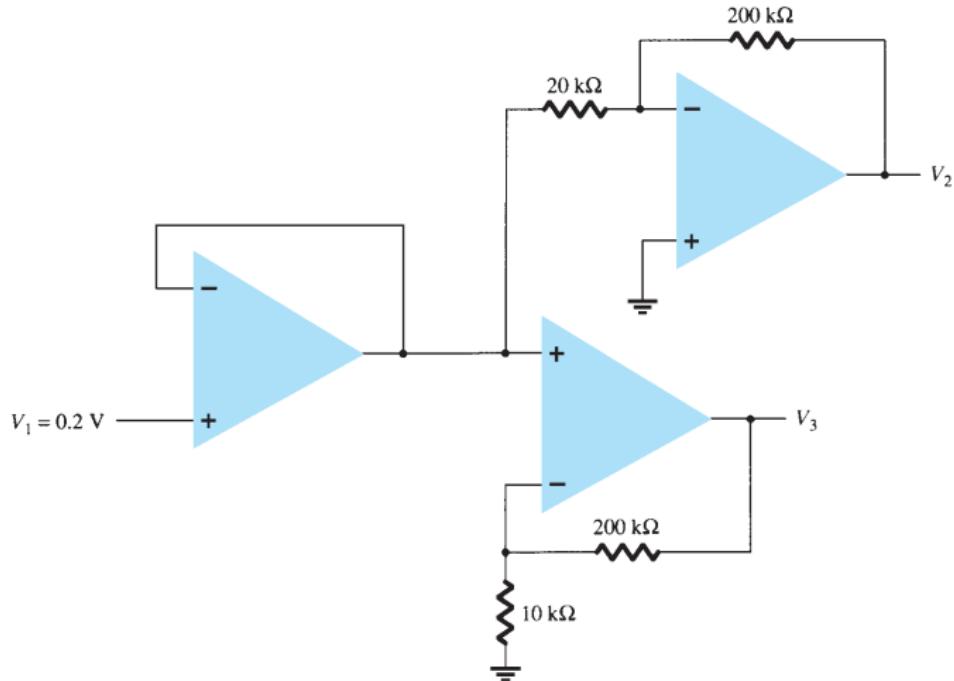


FIG. 10.72



Calculate the output voltage V_O developed by the circuit of Fig. 10.74.

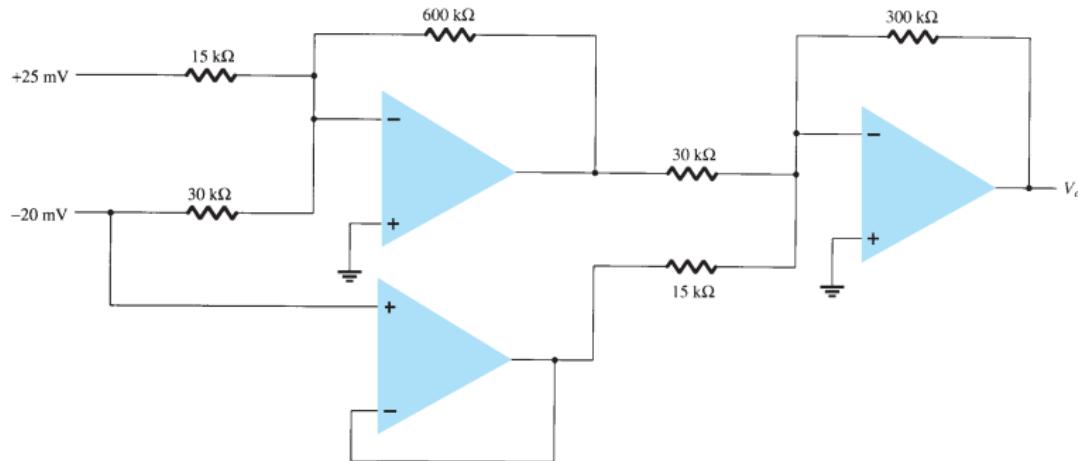


FIG. 10.74



Calculate the output voltage V_O in the circuit of Fig. 11.49.

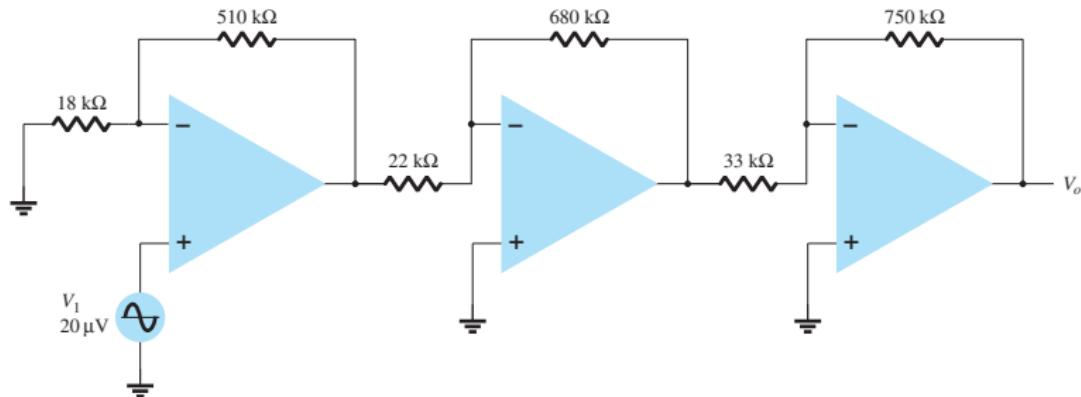


FIG. 11.49